

EE224 Digital Circuits-Project

IIT-B CPU

Table of Contents

Team Members.....	1
Finite State Machines for Instructions	1
ADD, ADC, ADZ.....	3
NDU, NDC, NDZ.....	4
ADI	5
LHI.....	6
LW.....	6
SW.....	7
LM.....	8
SM.....	9
BEQ.....	11
JAL.....	12
JLR.....	13
State Transition Table	14
State Diagram	15
DataPath	15

Team Members:

- Archit Gupta - 210100021
- Yashas M Salian - 210070095
- Ananya Chinmaya - 210070008
- Harsh Agarwal – 210070032

Finite State Machines for Instructions:**1. ADD, ADC, ADZ.****S1**

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S2

Operations	Control Signal
if(ins == 0001): IR(8-6) → RF_AD_OUT1 RF_DA_OUT1 → T1 elseif(ins == 0000 or ins == 0010 or ins == 1100): IR(8-6) → RF_AD_OUT_1 RF_DA_OUT 1 → T1 IR(11-9) → RF_AD_OUT_2 RF_DA_OUT_2 → T2 elseif(ins == 0100 or ins == 0101) IR(8-6) → RF_AD_OUT1 RD_DA_OUT1 → T1 IR(5-0) → SE16_6 → T2	T1_E T2_E

S3

Operations	Control Signal
T1 → ALU_A T2 → ALU_B ALU_C → T1	ADD T1_E

S4

Operations	Control Signal
If((C==0 && Z==0) (C==1 && Z==0 && Cen==1) (Z==1 && Zen ==1 && C==0)) { IR 5-3 → RF_AD_IN	RF_WR

T1 → RF_DA_IN }	
--------------------	--

2. NDU, NDC, NDZ

S1

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S2

Operations	Control Signal
if(ins == 0001): IR(8-6) → RF_AD_OUT1 RF_DA_OUT1 → T1 elseif(ins == 0000 or ins == 0010 or ins == 1100): IR(8-6) → RF_AD_OUT_1 RF_DA_OUT_1 → T1 IR(11-9) → RF_AD_OUT_2 RF_DA_OUT_2 → T2 elseif(ins == 0100 or ins == 0101) IR(8-6) → RF_AD_OUT1 RD_DA_OUT1 → T1 IR(5-0) → SE16_6 → T2	T1_E T2_E

S5:

Operations	Control Signal
T1 → ALU_A T2 → ALU_B ALU_C → T1	NAND T1_E

S4

Operations	Control Signal
If((C==0 && Z==0) (C==1&& Z==0&&Cen==1) (Z==1&&Zen ==1&&C==0)) { IR 5-3 → RF_AD_IN T1 → RF_DA_IN }	RF_WR

3. ADI**S1**

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S2

Operations	Control Signal
if(ins == 0001): IR(8-6)→ RF_AD_OUT1 RF_DA_OUT1 → T1 elseif(ins == 0000 or ins == 0010 or ins == 1100): IR(8-6)→ RF_AD_OUT_1 RF_DA_OUT 1→ T1 IR(11-9) → RF_AD_OUT_2 RF_DA_OUT_2 → T2 elseif(ins==0100 or ins==0101) IR(8-6) →RF_AD_OUT1 RD_DA_OUT1 → T1 IR(5-0) →SE16_6 → T2	T1_E T2_E

S3

Operations	Control Signal
T1 → ALU_A T2 → ALU_B ALU_C → T1	ADD T1_E

S6

Operations	Control Signal
$T1 \rightarrow RF_DA_IN$ $IR_{(8-6)} \rightarrow RF_AD_IN$	RF_WR

4. LHI**S1**

Operations	Control Signal
$RF_7 \rightarrow MEM_ADD$ $MEM_DATA \rightarrow IR$ $RF_7 \rightarrow ALU_A$ $+1 \rightarrow ALU_B$ $ALU_C \rightarrow RF_7$	MEM_RD RF_7 RF_WR IR_E ADD

S7

Operations	Control Signal
$IR_{(8-0)} \rightarrow SE16_9 \rightarrow T1$	T1_E

S8

Operations	Control Signal
$IR(11-9) \rightarrow RF_AD_IN$ $T1 \rightarrow RF_DA_IN$	RF_WR

5. LW**S1**

Operations	Control Signal
$R7 \rightarrow MEM_ADD$ $MEM_DATA \rightarrow IR$ $PC \rightarrow ALU_A$ $+1 \rightarrow ALU_B$ $ALU_C \rightarrow R7$	MEM_RD PC_E IR_E ADD

S2

Operations	Control Signal
if(ins == 0001): IR(8-6) → RF_AD_OUT1 RF_DA_OUT1 → T1 elseif(ins == 0000 or ins == 0010 or ins == 1100): IR(8-6) → RF_AD_OUT_1 RF_DA_OUT_1 → T1 IR(11-9) → RF_AD_OUT_2 RF_DA_OUT_2 → T2 elseif(ins == 0100 or ins == 0101) IR(8-6) → RF_AD_OUT1 RF_DA_OUT1 → T1 IR(5-0) → SE16_6 → T2	T1_E T2_E

S3

Operations	Control Signal
T1 → ALU_A T2 → ALU_B ALU_C → T1	ADD T1_E

S9

Operations	Control Signal
IR(11-9) → RF_AD_IN T1 → MEM_ADD MEM_DATA → RF_DA_IN	MEM_RD RF_W

6. SW**S1**

Operations	Control Signal
R7 → MEM_ADD MEM_DATA → IR PC → ALU_A +1 → ALU_B ALU_C → R7	MEM_RD PC_E IR_E ADD

S2

Operations	Control Signal
if(ins == 0001): IR(8-6) → RF_AD_OUT1 RF_DA_OUT1 → T1 elseif(ins == 0000 or ins == 0010 or ins == 1100): IR(8-6) → RF_AD_OUT_1 RF_DA_OUT_1 → T1 IR(11-9) → RF_AD_OUT_2 RF_DA_OUT_2 → T2 elseif(ins == 0100 or ins == 0101) IR(8-6) → RF_AD_OUT1 RF_DA_OUT1 → T1 IR(5-0) → SE16_6 → T2	T1_E T2_E

S3

Operations	Control Signal
T1 → ALU_A T2 → ALU_B ALU_C → T1	ADD T1_E

S10

Operations	Control Signal
IR(11-9) → RF_AD_OUT T1 → MEM_AD RF_DA_OUT → MEM_DATA	MEM_W

7. LM**S1**

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S18

Operations	Control Signal
IR(7-0) → Zero_Checker IF(Z=1) S1 Elseif(Z=0) S19	

S19

Operations	Control Signal
IR(7-0) → PEN_I PEN_O → RF_AD_IN IR(11-9) → RF_AD_OUT RF_DA_OUT → MEM_AD,T1 MEM_DATA → RF_DA_IN IR(7-0),PEN_O → LU_I LU-O → IR(7-0)	MEM_RD RF_WR IR_E

S20

Operations	Control Signal
T1 → ALU_A +1 → ALU_B IR(11-9) → RF_AD_IN ALU_C → RF_DA_IN	RF_WR IR_E ADD

Send to S18**8. SM****S1**

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S22

Operations	Control Signal
IR(7-0) → Zero_Checker IF(Z=1) S1 Elseif(Z=0) S21	MEM_RD T3_E

S21

Operations	Control Signal
IR(7-0) → PEN_I PEN_O → RF_AD_OUT1 IR(11-9) → RF_AD_OUT_2 RF_DA_OUT_2 → MEM_AD RF_DA_OUT1 → MEM_DATA IR(7-0), PEN_O → LU_I LU-O → IR(7-0)	MEM_WR IR_WR

S20

Operations	Control Signal
T1 → ALU_A +1 → ALU_B IR(11-9) → RF_AD_IN ALU_C → RF_DA_IN	RF_WR IR_E ADD

Send to S22

9. BEQ**S1**

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S2

Operations	Control Signal
if(ins == 0001): IR(8-6) → RF_AD_OUT1 RF_DA_OUT1 → T1 elseif(ins == 0000 or ins == 0010 or ins == 1100): IR(8-6) → RF_AD_OUT_1 RF_DA_OUT 1 → T1 IR(11-9) → RF_AD_OUT_2 RF_DA_OUT_2 → T2 elseif(ins == 0100 or ins == 0101) IR(8-6) → RF_AD_OUT1 RD_DA_OUT1 → T1 IR(5-0) → SE16_6 → T2	T1_E T2_E

S11

Operations	Control Signal
T1 → ALU.A T2 → ALU.B ALU.C → T1	SUB

IF Z=1 THEN**S12**

Operations	Control Signal
RF_7 → ALU.A +1 → ALU.B ALU.C → RF_7	SUB RF_WR

S13

Operations	Control Signal
IR(5-0)→SE16_6→ALU B RF_7→ALU.A ALU.C →RF_7	ADD RF_WR

10. JAL**S1**

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S12

Operations	Control Signal
RF_7→ALU A +1→ALU.B ALU.C →RF_7	SUB RF_WR

S14

Operations	Control Signal
IR(11-9) →RF_AD_IN RF_7 → RF_DA_IN	RF_W

S15

Operations	Control Signal
RF_7 → ALU_A IR(0-8) →SE16_9→ALU.B ALU.C→ RF_7	RF_W RF_S7 ADD

11. JLR**S1**

Operations	Control Signal
RF_7 → MEM_ADD MEM_DATA → IR RF_7 → ALU_A +1 → ALU_B ALU_C → RF_7	MEM_RD RF_7 RF_WR IR_E ADD

S16

Operations	Control Signal
RF_7 → ALU_A +1 → ALU_B IR(11-9) → RF_AD_IN ALU.C → RF_DA_IN	SUB RF_WR

S17

Operations	Control Signal
IR(8-6) → RF_AD_OUT RF_DA_OUT → RF_7_IN	RF_WR

State Transition Table

Current	Next	Condition
S1	S2	(!IR15 and !IR14 and !IR13 and !IR12) or (!IR15 and !IR14 and !IR13 and IR12) or (!IR15 and !IR14 and IR13 and !IR12) or (!IR15 and IR14 and !IR13 and !IR12) or (!IR15 and IR14 and !IR13 and IR12) or (IR15 and IR14 and !IR13 and !IR12)
S1	S7	!IR15 and !IR14 and IR13 and IR12
S1	S12	IR15 and !IR14 and !IR13 and !IR12
S1	S16	IR15 and !IR14 and !IR13 and IR12
S1	S18	!IR15 and IR14 and IR13 and !IR12
S1	S22	!IR15 and IR14 and IR13 and IR12
S2	S3	(!IR15 and !IR14 and !IR13 and !IR12) or (!IR15 and !IR14 and !IR13 and IR12) or (!IR15 and IR14 and !IR13 and !IR12) or (!IR15 and IR14 and !IR13 and IR12)
S2	S5	!IR15 and !IR14 and IR13 and !IR12
S2	S11	IR15 and IR14 and !IR13 and !IR12
S3	S4	!IR15 and !IR14 and !IR13 and !IR12
S3	S6	!IR15 and !IR14 and !IR13 and IR12
S3	S9	!IR15 and IR14 and !IR13 and !IR12
S3	S10	!IR15 and IR14 and !IR13 and IR12
S4	S1	unconditional
S5	S4	unconditional
S6	S1	unconditional
S7	S8	unconditional
S8	S1	unconditional
S9	S1	unconditional
S10	S1	unconditional
S11	S1	!Z
S11	S12	Z
S12	S13	IR15 and IR14 and !IR13 and !IR12
S12	S14	IR15 and !IR14 and !IR13 and !IR12
S13	S1	unconditional
S14	S15	unconditional
S15	S1	unconditional
S16	S17	unconditional
S17	S1	unconditional
S18	S1	Z
S18	S19	!Z
S19	S20	unconditional
S20	S18	!IR15 and IR14 and IR13 and !IR12
S20	S22	!IR15 and IR14 and IR13 and IR12
S22	S1	Z
S22	S21	!Z
S21	S20	unconditional

